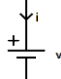
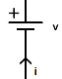




CHAPTER 1: BASIC CONCEPTS

<u>STANDARD SI PREFIXES</u>	10 ⁻¹²	10 ⁻⁹	10 ⁻⁶	10 ⁻³	10 ⁰	10 ³	10 ⁶	10 ⁹	10 ¹²
	pico (p)	nano (n)	micro (μ)	milli (m)		kilo (k)	mega (M)	giga (G)	tera (T)

BASIC ELECTRIC QUANTITIES

Quantity	Relationship	Unit
Current	$i(t) = \frac{dq(t)}{dt}$	Amperes (A)
Electric Charge	$q(t) = \int_{-\infty}^t i(x) dx$	Coulombs (C)
Voltage	$v = \frac{dw}{dq}$	Volts (V)
Power	$p = vi = \frac{dw}{dt}$	Watts (W)
Energy	$\Delta w = \int_{t_1}^{t_2} p dt = \int_{t_1}^{t_2} vi dt$	Joules (J)

<u>THE PASSIVE SIGN CONVENTION</u>	
$vi = +p \rightarrow$ power is absorbed 	$vi = -p \rightarrow$ power is Supplied 
<u>Tellegen's Theorem</u> $\rightarrow \Sigma p = 0 W$ in an electrical network	
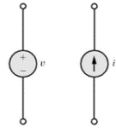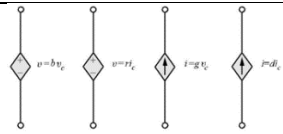
<u>ELECTRIC SOURCES</u>	 Independent Source: two terminal element that maintain a specified quantity (v or i).
	 Dependent or Controlled Sources: generate a quantity (v or i) determined by another quantity at specified location in the circuit.

CHAPTER 2: RESISTIVE CIRCUIT

<p><u>Ohm's Law</u> $V = IR$</p> <p>based on Ohm's law $\rightarrow P = VI = I^2R = \frac{V^2}{R}$</p>	
--	--

Kirchhoff's Laws	
Kirchhoff's Voltage Law (KVL)	Kirchhoff's Current Law (KCL)
$\sum_{j=1}^N v_j(t) = 0$ around any loop N: # of voltages in a loop EX: Single-loop circuit $\sum_{j=1}^3 V_j = 0 \Rightarrow -V_s + V_1 + V_2 = 0$	$\sum_{j=1}^N i_j(t) = 0$ @ any node, N: # of branches at a node EX: Single-node circuit $\sum_{j=1}^4 I_j = 0 \Rightarrow I_1 - I_2 + I_3 - I_4 = 0$

The Equivalent Resistance	
Series	Parallel
$R_s = R_1 + R_2 + R_3 + \dots$	$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots$

Y-Δ Transformation		
$R_a = \frac{R_1 R_2 + R_2 R_3 + R_1 R_3}{R_1}$ $R_b = \frac{R_1 R_2 + R_2 R_3 + R_1 R_3}{R_2}$ $R_c = \frac{R_1 R_2 + R_2 R_3 + R_1 R_3}{R_3}$		$R_1 = \frac{R_b R_c}{R_a + R_b + R_c}$ $R_2 = \frac{R_a R_c}{R_a + R_b + R_c}$ $R_3 = \frac{R_a R_b}{R_a + R_b + R_c}$
if $R_a = R_b = R_c$ & $R_1 = R_2 = R_3 \Rightarrow R_y = \frac{1}{3} R_\Delta$ & $R_\Delta = 3 R_y$		

Voltage Division Rule (VDR)

$$V_1 = V_s \frac{R_1}{R_1 + R_2}$$

$$V_2 = V_s \frac{R_2}{R_1 + R_2}$$

Current Division Rule (CDR)

$$I_1 = I_s \frac{R_2}{R_1 + R_2}$$

$$I_2 = I_s \frac{R_1}{R_1 + R_2}$$
Circuit with Dependent Source(s)

Procedures:

- STEP 1 Treat the dependent source as an independent source
- STEP 2 Apply KVL and/or KCL
- STEP 3 Specify its relationship to its controlling quantity

CHAPTER 3: NODAL & LOOP ANALYSIS TECHNIQUES


Nodal Analysis for an N-node Circuit

Procedures:

- STEP 1 Determine # of nodes (N) and choose a reference node (GN).
 STEP 2 Apply KCL to non GN nodes.
 STEP 3 Express currents in terms of node voltages.
 STEP 4 Solve for node voltages from the resulting N-1 eqn.

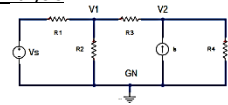Example of Nodal Analysis

N=3 @ V1, V2 and GN
 N-1= 3-1=2 linear eqn



$$\text{KCL @ V1 node: } \frac{V_1 - V_s}{R_1} + \frac{V_1}{R_2} + \frac{V_1 - V_2}{R_3} = 0$$

$$\text{KCL @ V2 node: } \frac{V_2 - V_1}{R_3} + \frac{V_2}{R_4} - I_s = 0$$

Nodal Analysis with Supernode

Supernode: a voltage source connected between two voltage nodes.

Procedures:


- STEP 1 Determine # of nodes (N) and choose a reference node (GN).
 STEP 2 Write a constraint eqn. for voltage source(s) (Nv) that forms supernode(s).
 STEP 3 Apply KCL to non GN nodes.
 STEP 4 Express currents in terms of node voltages.
 STEP 5 Solve for node voltages from the resulting N-1-Nv eqn.

Example of Nodal Analysis with a Supernode

N=3 @ V1, V2 and GN

Nv=1 (1 voltage source)

N-1-Nv=3-1-1= 1 linear eqn.

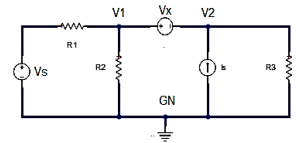

$$V_x = V_1 - V_2 \text{ (constraint eqn.)}$$

$$\text{KCL @ supernode: } \frac{V_1 - V_s}{R_1} + \frac{V_1}{R_2} + \frac{V_2}{R_3} - I_s = 0$$


Loop Analysis for an N-loop Circuit

Procedures:

- STEP 1 Determine # of meshes (M)
 STEP 2 Apply KVL to each mesh.
 STEP 3 Express voltages in terms of mesh currents.
 STEP 4 Solve for mesh currents from the resulting M eqn.

Example of Loop Analysis

M=2 Loops for I1 and I2
 M=2 linear eqn

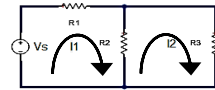

$$\text{KVL around Loop 1: } -V_s + R_1 I_1 + R_2 (I_1 - I_2) = 0$$

$$\text{KVL around Loop 2: } R_2 (I_2 - I_1) + R_3 I_2 = 0$$

Loop Analysis for an N-loop Circuit with Supermesh

Supermesh: a current source connected between two current loops.

Procedures:


- STEP 1 Determine # of meshes (M)
 STEP 2 Write a constraint eqn. for current source(s) (Mc) that forms supermesh(s).
 STEP 3 Apply KVL to each mesh.
 STEP 4 Express voltages in terms of mesh currents.
 STEP 5 Solve for mesh currents from the resulting M-Mc eqn.

Example of Loop Analysis

M=2 Loops for I1 and I2

Mc=1 (1 current source)



M-Mc=2-1=1 linear eqn.

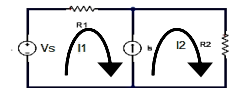



$$I_s = I_2 - I_1 \text{ (constraint eqn.)}$$



$$\text{KVL around Loop 1: } -V_s + R_1 I_1 + R_2 I_2 = 0$$

CHAPTER 4: OPERATIONAL AMPLIFIERS (Op-amp)

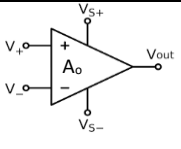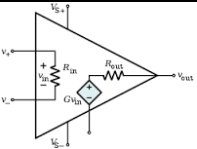Op-amp			
Model		Circuit	
	V_+ : noninverting input voltage V_- : inverting input voltage A_o (G): op-amp gain (Typically: 10^4 , 10^6) V_{out} : output voltage $V_{out} = A_o (V_+ - V_-)$		Op-amp is characterized by: <ul style="list-style-type: none"> - High R_{in} - Low R_{out} - Very high A_o

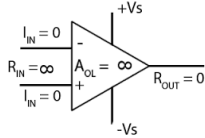Ideal Op-amp	
$V_+ = V_-$ $I_+ = I_- = 0$	

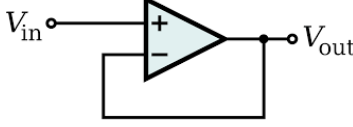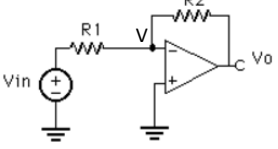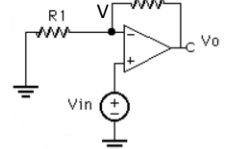Unity Gain Buffer	
$\frac{V_{out}}{V_{in}} = \frac{1}{1 + \frac{R_{in}}{A_o R_{in} + R_{out}}}$ $A_o \gg 1 \text{ and } R_{in} \gg R_{out} \Rightarrow \frac{V_{out}}{V_{in}} \approx 1$	

Solving Op-amp Circuit		
Procedures:	Inverting op-amp	Noninverting op-amp
		
	STEP 1 $V_+ = V_- = V = 0V$ STEP 2 Apply nodal analysis @ V $\frac{0 - V_{in}}{R_1} + \frac{0 - V_o}{R_2} = 0$ STEP 3 $V_o = -V_{in} \frac{R_2}{R_1}$ $A_v = \frac{V_o}{V_{in}} = -\frac{R_2}{R_1}$	STEP 1 $V_+ = V_- = V = V_{in}$ STEP 2 Apply nodal analysis @ V $\frac{V_{in}}{R_1} + \frac{V_{in} - V_o}{R_2} = 0$ STEP 3 $V_o = V_{in} \frac{R_1 + R_2}{R_1}$ $A_v = \frac{V_o}{V_{in}} = \frac{R_1 + R_2}{R_1}$

CHAPTER 5: ADDITIONAL ANALYSIS TECHNIQUES

Equivalence

Thevenin (th) Theorem

V_{th} is the open circuit voltage between A and B.

R_{th} is the resistance seen at AB where voltage source(s) is shorted and current source(s) is open.

$i = 0A \rightarrow V_{th} = V_{ab} = V \frac{R_2}{R_1 + R_2}$

$R_{th} = \frac{R_1 R_2}{R_1 + R_2} + R_3$

Linearity Property

Homogeneity (Scaling)	Additivity
$V = IR \rightarrow kV = kIR$	$V_1 = I_1 R \text{ \& } V_2 = I_2 R \rightarrow V_1 + V_2 = (I_1 + I_2) R$

Source Transformation

Interchange between Thevenin and Norton equivalent circuits.

Norton (N) Theorem

I_N is the open circuit voltage V_{AB} divide by R_{th} .

$R_N = R_{th}$

$I_N = \frac{V_{ab}}{R_N}$

$R_N = R_{th} = \frac{R_1 R_2}{R_1 + R_2} + R_3$

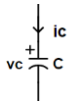
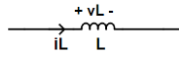
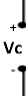
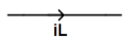
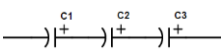

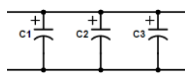
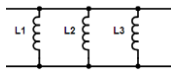
Maximum Power Transfer

$P_L = \frac{V_L^2}{R_L}$
 $V_L = V_s \frac{R_L}{R_L + R_s}$
 $R_L = R_s \rightarrow P_{Lmax} = \frac{V_s^2}{R_s} = \frac{V_s^2}{R_L}$

Superposition Theorem

STEP1: Pick a source and remove other: - voltage source: short circuit - current source: open circuit			
STEP 2: Determine individual solution	$I' = \frac{V_1}{R_1 + R_3}$	$I'' = -I_s \frac{R_3}{R_1 + R_3}$	$I''' = \frac{-V_2}{R_1 + R_3}$
STEP 3: Summate the individual solutions	$I = I' + I'' + I'''$		
<ul style="list-style-type: none"> # of sources = # of individual solution Not valid for nonlinear quantities i.e. power (P) 			

CHAPTER 6: CAPACITANCE and INDUCTANCE

	Capacitance (C)	Inductance (L)
<u>Symbol</u>		
<u>Unit</u>	Farad (F)	Henry (H)
<u>Main Relationships</u>	$i_c(t) = C \frac{dv_c(t)}{dt}$ $p(t) = C v_c(t) \frac{dv_c(t)}{dt}$ $w_c(t) = \frac{1}{2} C v_c^2(t)$	$v_L(t) = L \frac{di_L(t)}{dt}$ $p(t) = L i_L(t) \frac{di_L(t)}{dt}$ $w_L(t) = \frac{1}{2} L i_L^2(t)$
<u>DC Steady State</u>	Open circuit: $i_c(t) = 0$ 	Short circuit: $v_L(t) = 0$ 
<u>Series Combination</u>	$\frac{1}{C_s} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + \dots$ 	$L_s = L_1 + L_2 + L_3 + \dots$ 
<u>Parallel Combination</u>	$C_p = C_1 + C_2 + C_3 + \dots$ 	$\frac{1}{L_p} = \frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3} + \dots$ 
• Note: $v_c(t)$ and $i_L(t)$ cannot change instantaneously		

CHAPTER 7: 1ST AND 2ND ORDER TRANSIENT CIRCUITS1st Order Circuits

1st order differential equation $\rightarrow \frac{dx(t)}{dt} + ax(t) = f(t)$

Solution: $x(t) = x_p(t) + x_c(t) = k_1 + k_2 e^{-\frac{t}{\tau}}$, $\tau = \frac{1}{a}$


Particular/forced response $\rightarrow x_p(t) = k_1$

Complementary/natural response $\rightarrow x_c(t) = k_2 e^{-at}$


- Solution Procedures:

Step 1: Assume $v_o(t) = k_1 + k_2 e^{-\frac{t}{\tau}}$

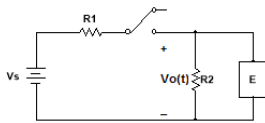
$$v_o(0^+) = k_1 + k_2, x(\infty) = k_1, \tau = \frac{L}{R_{eq}} = CR_{eq}$$



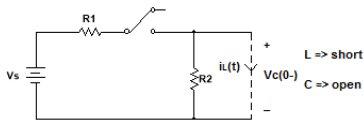
Step 2: Draw circuit before switch changes ($t = 0^-$), Solve $i_L(0^-)$ or $v_C(0^-)$.



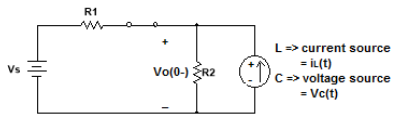
Step 3: Draw circuit after switch changes ($t = 0^+$), Solve $v_o(0^+)$.



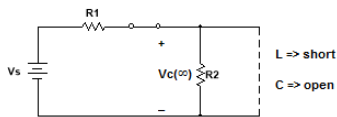Step 4: Draw circuit after switch changed ($t = \infty \approx 5\tau$), Solve $v_o(\infty)$.



Step 5: Draw circuit after switch changed ($t = \infty \approx 5\tau$), Solve R_{eq} with respect to storage element.

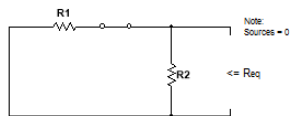2nd Order Circuits

2nd order differential equation $\rightarrow \frac{dx^2(t)}{dt^2} + a_1 \frac{dx(t)}{dt} + a_2 x(t) = 0$,

$$a_1 = 2\zeta \quad \text{and} \quad a_2 = \omega_o^2$$

ζ = damping ratio

ω_o = undamped natural frequency

- Solution Procedures:

Step 1: Write differential equation that describes circuit.

$$\frac{dx^2(t)}{dt^2} + a_1 \frac{dx(t)}{dt} + a_2 x(t) = 0$$

Step 2: Derive characteristic equation.

$$s^2 + 2\zeta\omega_o s + \omega_o^2 = 0$$

Step 3: Determine roots of the characteristic equation.

Step 4: Determine damping condition:

Case 1 – roots are real and unequal

$$\zeta > 1 = \text{overdamped}$$

$$\Rightarrow x(t) = k_1 e^{-(\zeta\omega_o - \sqrt{\zeta^2 - 1})t} + k_2 e^{-(\zeta\omega_o + \sqrt{\zeta^2 - 1})t}$$

Case 2 – roots are real and equal

$$\zeta = 1 = \text{critically damped}$$

$$\Rightarrow x(t) = B_1 e^{-\zeta\omega_o t} + B_2 t e^{-\zeta\omega_o t}$$

Case 3 – roots are complex

$$\zeta < 1 = \text{underdamped}$$

$$\Rightarrow x(t) = e^{-\zeta\omega_o t} (A_1 \cos(\omega_o \sqrt{1 - \zeta^2} t) + A_2 \sin(\omega_o \sqrt{1 - \zeta^2} t))$$

Step 5: Two initial conditions (given or derived) are used to obtain the two unknown coefficients in the response equation.

Chapter 8: AC Steady-State Analysis

Sinusoids

$$x(t) = X_m \sin(\omega t)$$

X_m = peak value/amplitude

ω = radian frequency (f) (rad/s)

$$f = \frac{1}{T} \text{ (Hz)}, T = \text{time (s)}$$

$$x_1(t) = X_1 \sin(\omega t + \theta_1)$$



$$\theta_1 = 0^\circ$$

$$x_2(t) = X_2 \sin(\omega t + \theta_2)$$

$\therefore x_1(t)$ "leads" $x_2(t)$ by θ_2


or $x_2(t)$ "lags" $x_1(t)$ by θ_2 , for $\theta_1 \neq \theta_2$

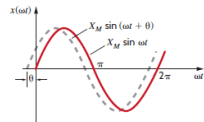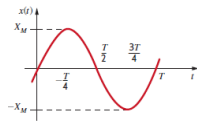If $\theta_1 = \theta_2$, $x_1(t)$ and $x_2(t)$ are "in phase".



Phase Diagrams

Resistor	Inductor	Capacitor
I is in phase with V	I lags V by 90°	I leads V by 90°

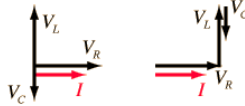

Waveform transforms

$$\cos(\omega t) = \sin(\omega t + 90^\circ)$$


$$\sin(\omega t) = \cos(\omega t - 90^\circ)$$

$$-\cos(\omega t) = \cos(\omega t \pm 180^\circ)$$


$$-\sin(\omega t) = \sin(\omega t \pm 180^\circ)$$

Domains

Time Domain

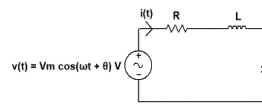


Frequency Domain

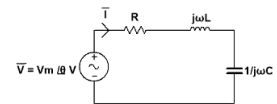


Impedance (Z) and Admittance (Y)

$$\bar{Z} = \frac{\bar{V}}{\bar{I}} = R \pm jX = \frac{V_m}{I_m} \angle \theta_V - \theta_I = Z \angle \theta_Z \text{ (}\Omega\text{)}$$
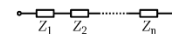
$$\bar{Z}_s = \bar{Z}_1 + \bar{Z}_2 + \dots + \bar{Z}_n$$


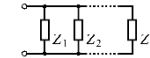
$$\frac{1}{\bar{Z}_p} = \frac{1}{\bar{Z}_1} + \frac{1}{\bar{Z}_2} + \dots + \frac{1}{\bar{Z}_n}$$



$$Z = \sqrt{R^2 + X^2}, \theta_Z = \tan^{-1} \frac{X}{R}$$



$$R = Z \cos \theta_Z, X = Z \sin \theta_Z$$

$$\bar{Y} = \frac{1}{\bar{Z}} = G + jB \text{ (S)}$$

$$\frac{1}{\bar{Y}_s} = \frac{1}{\bar{Y}_1} + \frac{1}{\bar{Y}_2} + \dots + \frac{1}{\bar{Y}_n}$$

$$\bar{Y}_p = \bar{Y}_1 + \bar{Y}_2 + \dots + \bar{Y}_n$$

AC Analysis

KVL: $\bar{V}_s = \bar{I}_1 \bar{Z}_1 + \bar{V}_1$


KCL: $\bar{I}_1 = \bar{I}_2 + \bar{I}_3$

Voltage Division:

$$\bar{V}_1 = \frac{\bar{V}_s (\bar{Z}_2 || \bar{Z}_3)}{\bar{Z}_1 + (\bar{Z}_2 || \bar{Z}_3)}$$

Current Division:

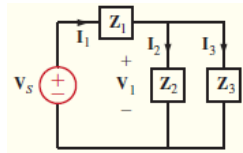
$$\bar{I}_2 = \frac{\bar{I}_1 (\bar{Z}_3)}{\bar{Z}_2 + \bar{Z}_3}$$



Nodal Analysis:

1) $\bar{V}_1 - \bar{V}_2 = \bar{V}_s$

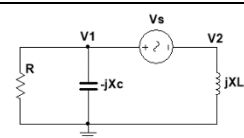
2) $\frac{\bar{V}_1}{R} + \frac{\bar{V}_1}{-jX_C} + \frac{\bar{V}_2}{jX_L} = 0$



Loop Analysis:

1) $\bar{I}_2 - \bar{I}_1 = \bar{I}_s$

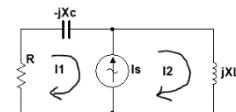2) $\bar{I}_1 (R - jX_C) + \bar{I}_2 (jX_L) = \bar{V}_s$



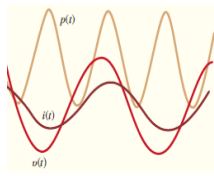
Other Analysis Techniques: Superposition, Source Exchange, Thévenin's Theorem, Norton's Theorem

CHAPTER 9: STEADY-STATE POWER ANALYSIS

Instantaneous power

$$p(t) = v(t)i(t) = V_m I_m \cos(\omega t + \theta_v) \cos(\omega t + \theta_i) \text{ W}$$

$$\Rightarrow p(t) = \underbrace{\left(\frac{V_m I_m}{2} \cos(\theta_v - \theta_i)\right)}_{\text{constant}} + \underbrace{\left(\frac{V_m I_m}{2} \cos(2\omega t + \theta_v + \theta_i)\right)}_{\text{double frequency}}$$

Average Power


$$P_{AVG} = \frac{V_m I_m}{2} \cos(\theta_v - \theta_i)$$

$$\therefore P_R = \frac{1}{2} V_m I_m \text{ W, and } P_L = P_C = 0 \text{ W}$$

Maximum Average Power Transfer


$$\bar{Z}_L = \bar{Z}_{TH}^* \text{ (i.e. } \bar{Z}_{TH} = R + jX \Rightarrow \bar{Z}_L = R - jX)$$

$$P_{max} = \frac{1}{2} I^2 R_{TH} = \frac{V_{TH}^2}{8R_{TH}}$$

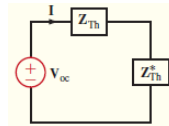Effective/RMS Values

$$I_{RMS} = \sqrt{\frac{1}{T} \int_0^T i^2(t) dt}$$

$$\text{Sinusoid: } I_{RMS} = \frac{I_m}{\sqrt{2}} \therefore P_R = I_{RMS}^2 R = \frac{V_{RMS}^2}{R}$$

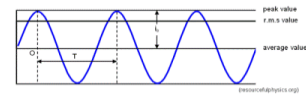
Complex Power

$$\bar{S} = \bar{V}_{RMS} \bar{I}_{RMS}^* = V_{RMS} I_{RMS} \angle(\theta_v - \theta_i) \text{ (VA)} = S \angle \theta_s = P + jQ$$

$$P = \text{Re}(\bar{S}) = V_{RMS} I_{RMS} \cos(\theta_v - \theta_i) \text{ (W)}$$

$$Q = \text{Im}(\bar{S}) = V_{RMS} I_{RMS} \sin(\theta_v - \theta_i) \text{ (VAR)}$$

(Note: +Q = inductor, -Q = capacitor)

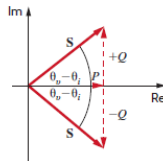
Power Factor

$$pf = \frac{P}{S} = \frac{P}{V_{RMS} I_{RMS}} = \cos(\theta_v - \theta_i) = \cos(\theta_c)$$

- Power Factor Correction

$$Q_{cap} = Q_{new} - Q_{old} = -j\omega C V_{RMS}^2$$

$$\therefore C = \frac{Q_{cap}}{\omega V_{RMS}^2}$$

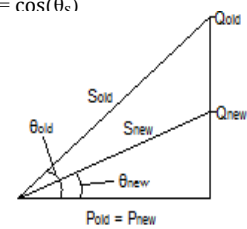Single-Phase Three-Wire Circuits



(Typical AC network in households)

$$\bar{V}_{an} = \bar{V}_{nb}$$

$$\text{If } \bar{Z}_{line,a} = \bar{Z}_{line,b}$$

$$\& \bar{Z}_{L,1} = \bar{Z}_{L,2} = \bar{Z}_{LL}$$

$$\Rightarrow \bar{I}_n = 0$$

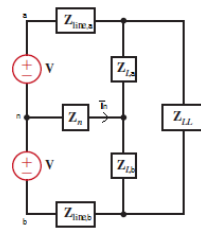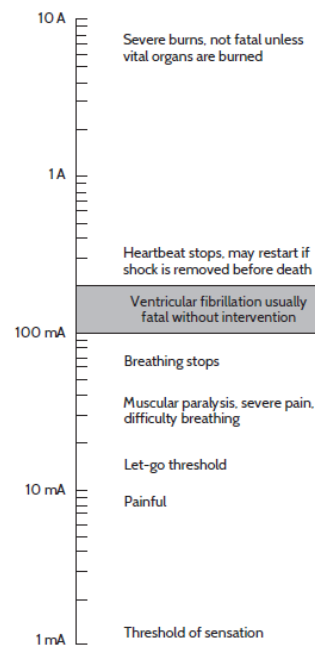Safety Considerations

CHAPTER 10: MAGNETICALLY COUPLED NETWORKS


Mutual Inductance

Dot notation – current $i_1(t)$ and $i_2(t)$:

BOTH entering or BOTH leaving $\Rightarrow +M$,


otherwise $\Rightarrow -M$

Examples:

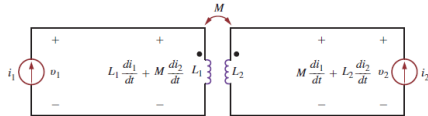

$$v_1(t) = L_1 \frac{di_1(t)}{dt} + M \frac{di_2(t)}{dt}$$
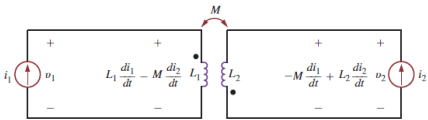
$$v_2(t) = M \frac{di_1(t)}{dt} + L_2 \frac{di_2(t)}{dt}$$



$$v_1(t) = L_1 \frac{di_1(t)}{dt} - M \frac{di_2(t)}{dt}$$

$$v_2(t) = -M \frac{di_1(t)}{dt} + L_2 \frac{di_2(t)}{dt}$$

Energy Analysis

$$w(t) = \frac{1}{2} L_1 [i_1(t)]^2 + \frac{1}{2} L_2 [i_2(t)]^2 \pm M i_1(t) i_2(t)$$


If $M \leq \sqrt{L_1 L_2}$, instantaneous energy stored is nonnegative.

Ideal Transformer

$$n = \frac{N_2}{N_1}$$


$$\frac{V_1}{V_2} = \frac{1}{n}$$

$$\frac{I_1}{I_2} = n$$

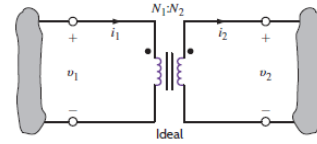


Impedance Reflection:


Example:

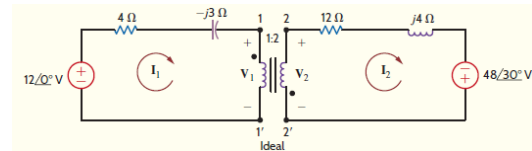

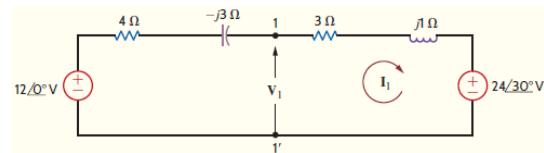Primary: $\bar{Z}_{1,eq} = \frac{Z_2}{n^2}$ and $\bar{V}_{1,eq} = \frac{V_{s,2}}{n}$





Secondary: $\bar{Z}_{2,eq} = n^2 \bar{Z}_1$ and $\bar{V}_{2,eq} = \frac{V_{s,1}}{n}$

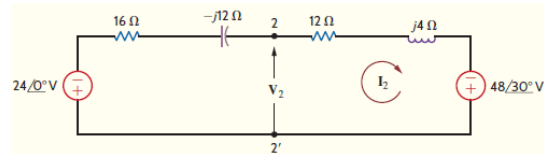

CHAPTER 11: POLYPHASERS CIRCUITS

Balanced three-phase (3 ϕ) quantities	
Frequency domain Representation	Time domain Representation
$A_{an} = A_{\text{peak}} \angle \theta$ $A_{bn} = A_{\text{peak}} \angle (\theta - 120^\circ)$ $A_{cn} = A_{\text{peak}} \angle (\theta + 120^\circ)$	$A_{an} = A_{\text{peak}} \cos(\theta)$ $A_{bn} = A_{\text{peak}} \cos(\theta - 120^\circ)$ $A_{cn} = A_{\text{peak}} \cos(\theta + 120^\circ)$
A: voltage (V) or current (I)	

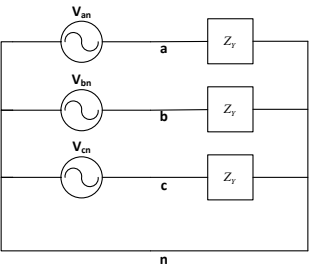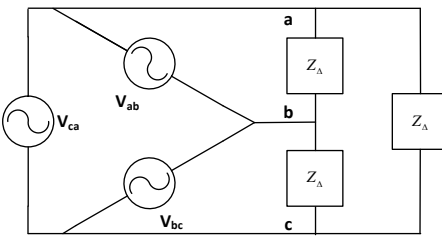Voltage, current, and impedance relationships for Y- Δ configurations	
Y connection	Δ connection
	
$V_{LL} = \sqrt{3}V_{LN} \angle \theta + 30^\circ$ (LL: line to line) (LN: line to neutral)	$V_L = V_P \angle \theta$ (L: line to line) (P: phase voltage)
$I_L = I_P \angle \theta$	$I_L = \sqrt{3}I_P \angle \theta + 30^\circ$
$I_n = I_a + I_b + I_c = 0$	$V_{ab} + V_{bc} + V_{ca} = 0$
$I_{LN} = \frac{V_{LN}}{Z_Y}$	$I_{LL} = \frac{V_{LL}}{Z_\Delta}$
$Z_Y = \frac{Z_\Delta}{3}$	$Z_\Delta = 3Z_Y$

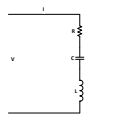
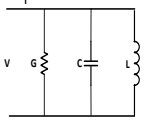
Power relationships in 3 ϕ circuits				
Real power	Reactive power	Complex power	Instantaneous power	Power factor
$P_T = 3P_P$ $= \sqrt{3}V_L I_L \cos \theta$ P _P : 1 ϕ real power P _T : 3 ϕ real power L: line	$Q_T = 3Q_P$ $= \sqrt{3}V_L I_L \sin \theta$ Q _P : 1 ϕ reactive power Q _T : 3 ϕ reactive power L: line	$S_T = P_T + jQ_T$ S _T : 3 ϕ complex power	$p(t) = 3 \frac{V_m I_m}{2} \cos \theta \text{ W}$ V _m : maximum voltage I _m : maximum current	$pf = \frac{P_T}{S_T}$ $= \cos(\theta_V - \theta_I)$ θ_V : voltage phase angel θ_I : current phase angel

CHAPTER 12: VARIABLE-FREQUENCY NETWORK PERFORMANCE









Network transfer functions		
Input	output	Transfer function
Voltage	Voltage	Voltage gain $G_v(j\omega)$
Current	Voltage	Transimpedance $Z(j\omega)$
Current	Current	Current gain $G_i(j\omega)$
Voltage	Current	Transadmittance $Y(j\omega)$

Network function		
$H(j\omega) = H(s) = \frac{N(s)}{D(s)} = K \frac{(s - z_1)(s - z_2) \dots (s - z_m)}{(s - p_1)(s - p_2) \dots (s - p_n)}$		
K : constant	z_m : zeros of $H(s)$	p_n : poles of $H(s)$
$s = z_1 \text{ or } z_2 \dots, z_m \rightarrow H(s) = 0$		
$s = p_1 \text{ or } p_2 \dots, p_n \rightarrow H(s) = \infty$		

Bode plot Basics		
$H(j\omega) = K \frac{(j\omega - z_1)(j\omega - z_2) \dots}{(j\omega - p_1)(j\omega - p_2) \dots}$ (standard form)		
Decibels (dB) = $20 \log \frac{V_{out}}{V_{in}} = 10 \log \left(\frac{V_{out}}{V_{in}} \right)^2 = 10 \log \frac{P_{out}}{P_{in}}$		
Bode plots	1. Magnitude ($20 \log H(j\omega) $ dB) vs ω (rad/s)	2. phase angle ($\angle H(j\omega)$) vs. ω (rad/s)
Magnitude in dB	$20 \log H(j\omega) = 20 \log K + 20 \log j\omega - z_1 + 20 \log j\omega - z_2 + \dots - 20 \log j\omega - p_1 - 20 \log j\omega - p_2 - \dots$	
Phase angle	$\angle H(j\omega) = \angle K + \angle(j\omega - z_1) + \angle(j\omega - z_2) + \dots - \angle(j\omega - p_1) - \angle(j\omega - p_2) - \dots$	
Sketch bode plot	STEP 1 Rewrite the transfer function (TF) in Standard form. STEP 2 Separate the TF into its constituent parts and find corner frequency (ω_r) i.e. z_1, z_2, p_1, p_2 STEP 3 Draw the magnitude plot @ each ω_r by +20dB/dec for a zero and -20dB/dec for a pole. STEP 4 Calculate the phase angle @ each ω_r and draw the resulting phase plot.	

Resonance	
Circuit topology	
Series resonance	Parallel resonance
	
Impedance	Admittance
$Z(j\omega) = R + j\omega L + \frac{1}{j\omega C}$	$Y(j\omega) = G + j\omega C + \frac{1}{j\omega L}$
Quality factor	
$Q = \frac{\omega_0 L}{R} = \frac{1}{\omega_0 C R} = \frac{1}{R} \sqrt{\frac{L}{C}}$	$Q = \frac{R}{\omega_0 L} = \frac{1}{G \omega_0 L} = R \omega_0 C = \frac{\omega_0 C}{G}$
Resonant frequency	
$\omega_0 = \frac{1}{\sqrt{LC}}$	
Bandwidth	
$\omega_{H\omega} - \omega_{L\omega} = \frac{R}{L}$	$\omega_{H\omega} - \omega_{L\omega} = \frac{1}{RC}$

Scaling a circuit			
	Resistor	Inductor	Capacitor
Magnitude scaling	$R \rightarrow K_M R$	$L \rightarrow K_M L$	$C \rightarrow \frac{C}{K_M}$
Frequency scaling	$R \rightarrow R$	$L \rightarrow \frac{L}{K_f}$	$C \rightarrow \frac{C}{K_f}$

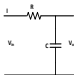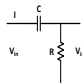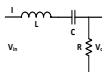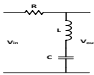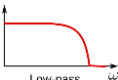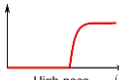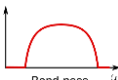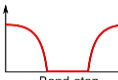Passive Filters			
High-pass filter	Low-pass filter	Band-pass filter	Band-reject filter
			
Magnitude response			
 Low-pass ω	 High-pass ω	 Band-pass ω	 Band-stop ω
Transfer functions			
$G_c(j\omega) = \frac{1}{1 + j\omega RC}$	$G_c(j\omega) = \frac{j\omega RC}{1 + j\omega RC}$	$G_c(j\omega) = \frac{R}{1 + j(\omega L - 1/\omega C)}$	
Magnitude			
$M(\omega) = \frac{1}{\sqrt{1 + (\omega\tau)^2}}$ Time constant $\tau = RC$	$M(\omega) = \frac{\omega\tau}{\sqrt{1 + (\omega\tau)^2}}$	$M(\omega) = \frac{RC\omega}{\sqrt{(RC\omega)^2 + (\omega^2 LC - 1)^2}}$	
Phase angle		Bandwidth	
$\phi(\omega) = -\tan^{-1}\omega\tau$	$\phi(\omega) = \frac{\pi}{2} - \tan^{-1}\omega\tau$	$BW = \frac{R}{L}$	

CHAPTER 13: THE LAPLACE TRANSFORM

Basics	
Laplace transform	$\mathcal{L}[f(t)] = F(s) = \int_0^{\infty} f(t)e^{-st} dt$
Inverse Laplace transform	$\mathcal{L}^{-1}[F(s)] = f(t) = \frac{1}{2\pi j} \int_{\sigma-jw}^{\sigma+jw} F(s)e^{st} dt$
$s = \sigma + jw$	
Unit impulse	$\int_{t_1}^{t_2} f(t) \delta(t - t_0) dt = \begin{cases} f(t_0) & t_1 < t_0 < t_2 \\ 0 & t_0 < t_1, t_0 > t_2 \end{cases}$

Laplace Transform Pairs	
$f(t)$	$F(s)$
$\delta(t)$	1
$u(t)$	$\frac{1}{s}$
e^{-at}	$\frac{1}{s+a}$
t	$\frac{1}{s^2}$
$\frac{t^n}{n!}$	$\frac{1}{s^{n+1}}$
te^{-at}	$\frac{1}{(s+a)^2}$
$\frac{t^n e^{-at}}{n!}$	$\frac{1}{(s+a)^{n+1}}$
$\sin bt$	$\frac{b}{s^2 + b^2}$
$\cos bt$	$\frac{s}{s^2 + b^2}$
$e^{-at} \sin bt$	$\frac{b}{(s+a)^2 + b^2}$
$e^{-at} \cos bt$	$\frac{s+a}{(s+a)^2 + b^2}$

Laplace Transform Properties		
Property	$f(t)$	$F(s)$
Magnitude scaling	$Af(t)$	$AF(s)$
Addition/subtraction	$f_1(t) \pm f_2(t)$	$F_1(s) \pm F_2(s)$
Time scaling	$f(at)$	$\frac{1}{a} F\left(\frac{s}{a}\right), a > 0$
Time shifting	$f(t-t_0)u(t-t_0), t \geq 0$	$e^{-ts} F(s)$
	$f(t)u(t-t_0), t \geq 0$	$e^{-ts} \mathcal{L}[f(t+t_0)]$
Frequency shifting	$e^{-at} f(t)$	$F(s+a)$
Differentiation	$\frac{d^n f(t)}{dt^n}$	$s^n F(s) - s^{n-1} f(0) - s^{n-2} f'(0) \cdots - s f^{(n-1)}(0)$
Multiplication by t	$tf(t)$	$-\frac{d^n f(s)}{ds^n}$
	$t^n f(t)$	$(-1)^n \frac{d^n f(s)}{ds^n}$
division by t	$\frac{f(t)}{t}$	$\int_s^{\infty} F(\lambda) d\lambda$
Integration	$\int_0^t f(\lambda) d\lambda$	$\frac{1}{s} F(s)$
Convolution	$\int_0^t f_1(\lambda) f_2(t-\lambda) d\lambda$	$F_1(s) F_2(s)$
Initial-value theorems	$\lim_{t \rightarrow 0^+} f(t)$	$\lim_{s \rightarrow \infty} sF(s)$
Final-value theorems	$\lim_{t \rightarrow \infty} f(t)$	$\lim_{s \rightarrow 0} sF(s)$

CHAPTER 14: APPLICATION OF THE LAPLACE TRANSFORM TO CIRCUIT ANALYSIS


Circuit Element Models

Resistor (R) in s-domain	Inductor (L) in s-domain	Capacitor (C) in s-domain
$R \rightarrow R \quad V(s) = RI(s)$	$L \rightarrow sL \begin{cases} V(s) = sLI(s) - Li(0) \\ I(s) = \frac{V(s)}{sL} + \frac{i(0)}{s} \end{cases}$	$C \rightarrow \frac{1}{sC} \begin{cases} V(s) = \frac{I(s)}{sC} + \frac{v(0)}{s} \\ I(s) = sCV(s) - Cv(0) \end{cases}$


Laplace Circuit Solution

Procedures:

- STEP 1 Solve for initial capacitor voltages and inductor currents.
- STEP 2 Draw the circuit at $t < 0$, replace the capacitor with an open circuit and inductor with a short circuit.
- STEP 3 Draw an s-domain circuit by substituting an s-domain representation for all circuit elements.
- STEP 4 Use circuit analysis to solve for the appropriate voltage and/or current.
- STEP 5 Perform the inverse Laplace transform to convert the voltage and/or current back to the time domain.

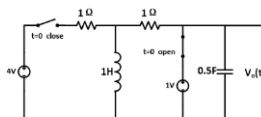Example


- Solve for initial conditions

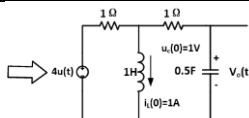

$V_c(0) = 1V$

$I_L(0) = 1A$

- Convert to s-domain

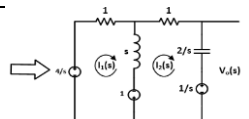2- Solve for $V_o(s)$

$$V_o(s) = \frac{2}{s} I_2(2) + \frac{1}{s} = \frac{s + 3.5}{s^2 + 1.5s + 1}$$

3- Convert to time domain

$$v_o(t) = \left[4.29e^{-0.75t} \cos\left(\frac{\sqrt{7}}{4}t - 76.5^\circ\right) \right] u(t) \text{ V}$$

1- Apply mesh analysis to find I_1 and I_2

$$(s+1)I_1(s) - sI_2(s) = \frac{4}{s} + 1$$

$$-sI_1(s) + \left(s + \frac{2}{s} + 1\right)I_2(s) = \frac{-1}{s} - 1$$

$$I_1(s) = \frac{4s^2 + 6s + 8}{s(2s^2 + 3s + 2)}$$

$$I_2(s) = \frac{2s - 1}{2s^2 + 3s + 2}$$

Steady-State Response

$$\mathbf{Y}(s) = \mathbf{H}(s)\mathbf{X}(s)$$

Transient comes from the poles of $\mathbf{H}(s)$ & Steady-state portion comes from the poles of $\mathbf{X}(s)$ The steady-state response: X_M is the maximum of $\mathbf{X}(s)$

$$y_{ss}(t) = X_M |H(j\omega_0)| \cos[\omega_0 t + \phi(j\omega_0)]$$

CHAPTER 15: FOURIER ANALYSIS TECHNIQUES

Fourier Series

$$f(t) = f(t + nT_0) \quad n = \pm 1, \pm 2, \pm 3 \dots \Leftrightarrow f(t) = a_0 + \sum_{n=1}^{\infty} D_n \cos(n\omega_0 t + \theta_n)$$

Exponential Fourier series

$$f(t) = \sum_{n=-\infty}^{\infty} c_n e^{jn\omega_0 t}$$

$$c_n = \frac{1}{T_0} \int_{t_1}^{t_1+T_0} f(t) e^{-jn\omega_0 t} dt$$

Trigonometric Fourier series

$$f(t) = a_0 + \sum_{n=1}^{\infty} (a_n \cos n\omega_0 t + b_n \sin n\omega_0 t)$$

$$a_n = \frac{2}{T_0} \int_{t_1}^{t_1+T_0} f(t) \cos n\omega_0 t dt \quad b_n = \frac{2}{T_0} \int_{t_1}^{t_1+T_0} f(t) \sin n\omega_0 t dt$$

Types Trigonometric Fourier seriesEven-function symmetry

$$f(t) = f(-t)$$

$$a_n = \frac{4}{T_0} \int_0^{T_0/2} f(t) \cos n\omega_0 t dt$$

$$b_n = 0$$

$$a_0 = \frac{2}{T_0} \int_0^{T_0/2} f(t) dt$$

Odd-function symmetry

$$f(t) = -f(-t)$$

$$a_n = 0 \quad \text{for all } n > 0$$

$$b_n = \frac{4}{T_0} \int_0^{T_0/2} f(t) \sin n\omega_0 t dt$$

$$a_0 = 0$$

Half-wave symmetry

$$f(t) = -f\left(t - \frac{T_0}{2}\right)$$

n even

$$a_n = 0$$

$$b_n = 0$$

n odd

$$a_n = \frac{4}{T_0} \int_0^{T_0/2} f(t) \cos n\omega_0 t dt$$

$$b_n = \frac{4}{T_0} \int_0^{T_0/2} f(t) \sin n\omega_0 t dt$$

$$a_0 = 0$$

Average Power

$$P = V_{DC} I_{DC} + \sum_{n=1}^{\infty} \frac{V_n I_n}{2} \cos(\theta_{v_n} - \theta_{i_n})$$

Fourier Transform

$$F(\omega) = \int_{-\infty}^{\infty} f(t) e^{-j\omega t} dt \quad f(t) = \frac{1}{2\pi} \int_{-\infty}^{\infty} F(\omega) e^{j\omega t} d\omega$$

Fourier Transform Pairs

$f(t)$	$F(\omega)$
$\mathcal{F}^{-1}[F(\omega)] = \frac{1}{2\pi} \int_{-\infty}^{\infty} F(\omega) e^{j\omega t} d\omega$	$\mathcal{F}[f(t)] = \int_{-\infty}^{\infty} f(t) e^{-j\omega t} dt$
$\delta(t-a)$	$e^{-j\omega a}$
A	$2\pi A \delta(\omega)$
$e^{j\omega_0 t}$	$2\pi \delta(\omega - \omega_0)$
$\cos \omega_0 t$	$\pi \delta(\omega - \omega_0) + \pi \delta(\omega + \omega_0)$
$\sin \omega_0 t$	$j\pi \delta(\omega + \omega_0) - j\pi \delta(\omega - \omega_0)$
$e^{-at} u(t), a > 0$	$\frac{1}{a + j\omega}$
$e^{- a t}, a > 0$	$\frac{2a}{a^2 + \omega^2}$
$e^{-at} \cos \omega_0 t u(t), a > 0$	$\frac{j\omega + a}{(j\omega + a)^2 + \omega_0^2}$
$e^{-at} \sin \omega_0 t u(t), a > 0$	$\frac{\omega_0}{(j\omega + a)^2 + \omega_0^2}$

Fourier Transform Properties

Linearity	$Af(t)$	$AF(\omega)$
Addition/subtraction	$f_1(t) \pm f_2(t)$	$F_1(\omega) \pm F_2(\omega)$
Time-scaling	$f(at)$	$\frac{1}{ a } F\left(\frac{\omega}{a}\right), a > 0$
Time-shifting	$f(t-t_0)$	$e^{-j\omega t_0} F(\omega)$
modulation	$e^{j\omega_0 t} f(t)$	$F(\omega - \omega_0)$
differentiation	$\frac{d^n f(t)}{dt^n}$	$(j\omega)^n F(\omega)$
Multiplication by t	$t^n f(t)$	$(j)^n \frac{d^n F(\omega)}{d\omega^n}$
convolution	$\int_{-\infty}^{\infty} f_1(x) f_2(t-x) dx$	$F_1(\omega) F_2(\omega)$
	$f_1(t) f_2(t)$	$\frac{1}{2\pi} \int_{-\infty}^{\infty} F_1(x) F_2(\omega-x) dx$
Parseval's Theorem	$\int_{-\infty}^{\infty} f^2(t) dt$	$\frac{1}{2\pi} \int_{-\infty}^{\infty} F(\omega) ^2 d\omega$

CHAPTER 15: FOURIER ANALYSIS TECHNIQUES

Fourier series $f(t) = f(t + nT_0) \quad n = \pm 1, \pm 2, \pm 3, \dots \Leftrightarrow f(t) = a_0 + \sum_{n=1}^{\infty} D_n \cos(n\omega_0 t + \theta_n) \quad \text{where } \omega_0 = \frac{2\pi}{T_0}$

Exponential Fourier series	Trigonometric Fourier series
$f(t) = \sum_{n=-\infty}^{\infty} c_n e^{jn\omega_0 t}$	$f(t) = a_0 + \sum_{n=1}^{\infty} (a_n \cos n\omega_0 t + b_n \sin n\omega_0 t)$
$c_n = \frac{1}{T_0} \int_{t_0}^{t_0+T_0} f(t) e^{-jn\omega_0 t} dt$	$a_n = \frac{2}{T_0} \int_{t_0}^{t_0+T_0} f(t) \cos n\omega_0 t dt \quad b_n = \frac{2}{T_0} \int_{t_0}^{t_0+T_0} f(t) \sin n\omega_0 t dt$

Special situation for trigonometric Fourier series

Even-function symmetry $f(t) = f(-t)$	Odd-function symmetry $f(t) = -f(-t)$	Half-wave symmetry $f(t) = -f\left(t - \frac{T_0}{2}\right)$	
		n even	n odd
$a_n = \frac{4}{T_0} \int_0^{T_0/2} f(t) \cos n\omega_0 t dt$	$a_n = 0 \quad \text{for all } n > 0$	$a_n = 0$	$a_n = \frac{4}{T_0} \int_0^{T_0/2} f(t) \cos n\omega_0 t dt$
$b_n = 0$	$b_n = \frac{4}{T_0} \int_0^{T_0/2} f(t) \sin n\omega_0 t dt$	$b_n = 0$	$b_n = \frac{4}{T_0} \int_0^{T_0/2} f(t) \sin n\omega_0 t dt$
$a_0 = \frac{2}{T_0} \int_0^{T_0/2} f(t) dt$	$a_0 = 0$	$a_0 = 0$	

Average power

$$P = V_{DC} I_{DC} + \sum_{n=1}^{\infty} \frac{V_n I_n}{2} \cos(\theta_{v_n} - \theta_{i_n})$$

Fourier transform pair

$f(t)$	$F(\omega)$
$F^{-1}[F(\omega)] = \frac{1}{2\pi} \int_{-\infty}^{\infty} F(\omega) e^{j\omega t} d\omega$	$F[f(t)] = \int_{-\infty}^{\infty} f(t) e^{-j\omega t} dt$
$\delta(t-a)$	$e^{-j\omega a}$
A	$2\pi A \delta(\omega)$
$e^{j\omega_0 t}$	$2\pi \delta(\omega - \omega_0)$
$\cos \omega_0 t$	$\pi \delta(\omega - \omega_0) + \pi \delta(\omega + \omega_0)$
$\sin \omega_0 t$	$j\pi \delta(\omega + \omega_0) - j\pi \delta(\omega - \omega_0)$
$e^{-at} u(t), a > 0$	$\frac{1}{a + j\omega}$
$e^{-\frac{1}{a}t} u(t), a > 0$	$\frac{2a}{a^2 + \omega^2}$
$e^{-at} \cos \omega_0 t u(t), a > 0$	$\frac{j\omega + a}{(j\omega + a)^2 + \omega_0^2}$
$e^{-at} \sin \omega_0 t u(t), a > 0$	$\frac{\omega_0}{(j\omega + a)^2 + \omega_0^2}$

Property of Fourier's transform

Property	$f(t)$	$F(\omega)$
Linearity	$Af(t)$	$AF(\omega)$
Addition/subtraction	$f_1(t) \pm f_2(t)$	$F_1(\omega) \pm F_2(\omega)$
Time-scaling	$f(at)$	$\frac{1}{a} F\left(\frac{\omega}{a}\right), a > 0$
Time-shifting	$f(t - t_0)$	$e^{-j\omega t_0} F(\omega)$
modulation	$e^{j\omega_0 t} f(t)$	$F(\omega - \omega_0)$
differentiation	$\frac{d^n f(t)}{dt^n}$	$(j\omega)^n F(\omega)$
Multiplication by t	$t^n f(t)$	$(j)^n \frac{d^n F(\omega)}{d\omega^n}$
convolution	$\int_{-\infty}^{\infty} f_1(x) f_2(t-x) dx$	$F_1(\omega) F_2(\omega)$
	$f_1(t) f_2(t)$	$\frac{1}{2\pi} \int_{-\infty}^{\infty} F_1(x) F_2(\omega-x) dx$

Fourier transform for an aperiodic function

$$F(\omega) = \int_{-\infty}^{\infty} f(t) e^{-j\omega t} dt$$

$$f(t) = \frac{1}{2\pi} \int_{-\infty}^{\infty} F(\omega) e^{j\omega t} d\omega$$

Parseval's Theorem

$$\int_{-\infty}^{\infty} f^2(t) dt = \frac{1}{2\pi} \int_{-\infty}^{\infty} |F(\omega)|^2 d\omega$$