

Lab Final: Part 2

Brandon Eidson
Revised by Elizabeth Devore
July 2016

You may not collaborate with other students on this project. If it is discovered that you gave assistance to or received assistance from another student, you will automatically receive a grade of 0 for part 1 and part 2 of the lab final.

A location in the power system can be modeled by the circuit in Figure 1. The line is modeled as a resistor and the load is modeled by a series resistance and inductance. The systems details are as follows:

- $v_s(t) = 5\cos(628.32t + \theta_{v_s})$ V (Set the function generator, FGEN, to output this voltage; your actual output will not perfectly match this.)
- $R_{\text{LINE}} \approx 10 \Omega$
- $R_{\text{LOAD}} \approx 330 \Omega$
- $L \approx 0.4$ H

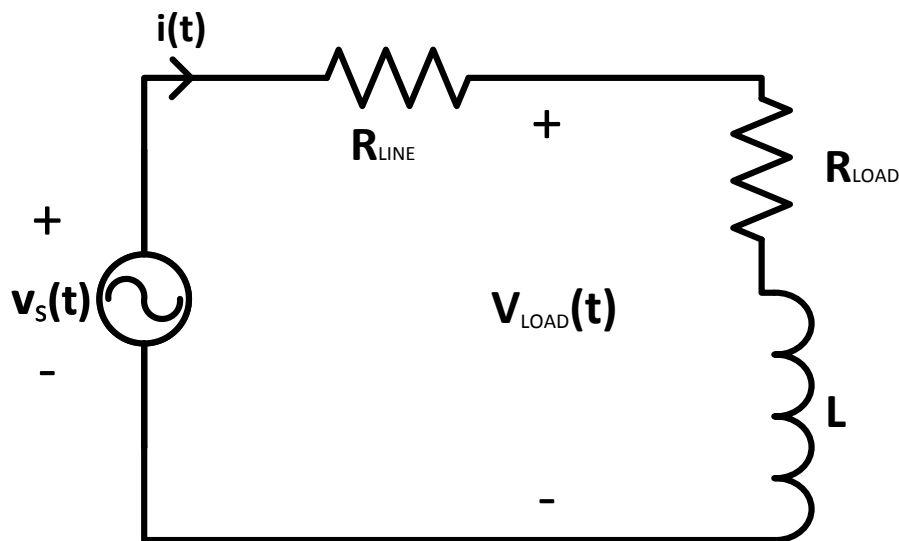


Figure 1: Power System Model

You have been assigned to choose a capacitor to insert in parallel with the load (see Figure 2) to adjust the load's power factor to within the following limits:

- $0.970 \leq \text{pf} \leq 0.990$ lagging

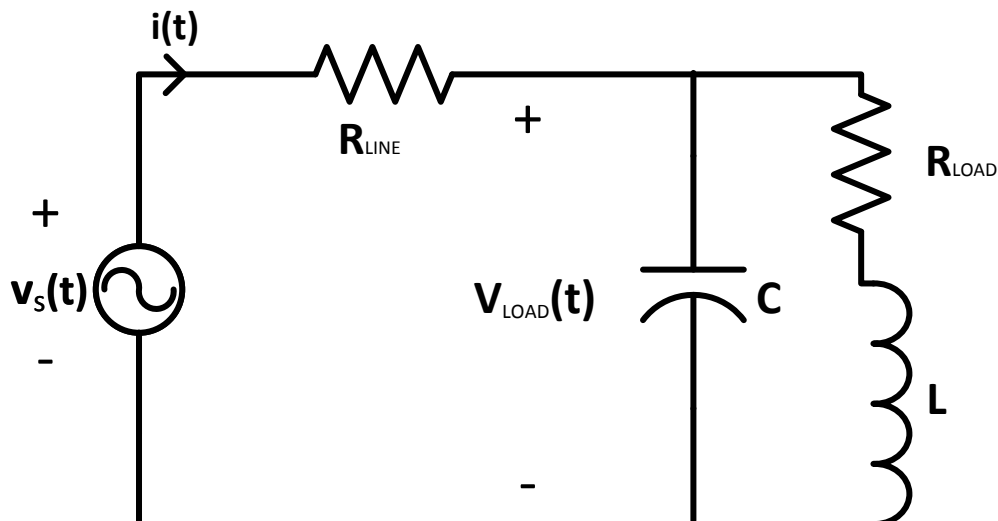


Figure 2: Power System Model for pf Correction

Your grade is dependent on the following (no lab report is required):

- Successful design of C.
- Successful justification to the T.A. of your selection of C (via measurements of R-L circuit, mathematics, simulation, and/or answering your T.A.'s verbal questions - DO NOT USE MULTISIM AS A TRAIL AND ERROR ONLY).
- Successful construction of your design using the NI ELVIS lab equipment.
- Successful demonstration of the operation of your design using the NI ELVIS oscilloscope and necessary calculations using the oscilloscope's measurement(s) to prove you've met the requirements for pf.

You are not permitted to use the theoretical values for $v_s(t)$, R_{LINE} , R_{LOAD} , or L in the justification of your design. Only measured values can be used.

Design Hints:

- Treat the phase on the source voltage, θ_{v_s} , as 0° .
- You may combine multiple capacitors to build the C you use in your breadboarded circuit. However, you may not use more than four capacitors.
- The sequence of measurements and calculations from Experiment #12 will serve as a helpful reference.